

# Template Week 2 – Logic

Student number:

**578848**

## Assignment 2.1: Parking lot

Which gates do you need?

**Three-Input AND gate (Or two two-input AND gates)**

Complete this table

| Parking lot 1 | Parking lot 2 | Parking lot 3 | Result (full) |
|---------------|---------------|---------------|---------------|
| 0             | 0             | 0             | 0             |
| 0             | 0             | 1             | 0             |
| 0             | 1             | 0             | 0             |
| 1             | 0             | 0             | 0             |
| 1             | 1             | 0             | 0             |
| 0             | 1             | 1             | 0             |
| 1             | 0             | 1             | 0             |
| 1             | 1             | 1             | 1             |

Basically every row that has zero in it, would yield 0 and only row with all ones would yield 1.

## Assignment 2.2: Android or iPhone

Which gates do you need?

**I need one XOR gate.**

Complete this table

| Android phone | iPhone | Result (Phone in possession) |
|---------------|--------|------------------------------|
| 0             | 0      | 0                            |
| 1             | 1      | 0                            |
| 1             | 0      | 1                            |
| 0             | 1      | 1                            |

### Assignment 2.3: Four NAND gates

Complete this table


| A | B | Q |
|---|---|---|
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 0 |
| 0 | 0 | 1 |

How can the design be simplified?

You could use AND gate for A and B and then NOT gate to get the same result.
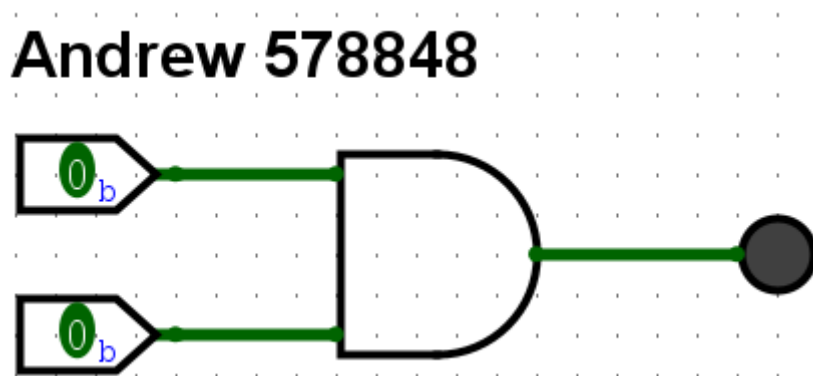
### Assignment 2.4: Getting to know Logisim evolution


Screenshot of the design with your name and student number in it:



### Assignment 2.5: SR Latch

Screenshot SR Latch in Logisim with your name and student number:


Andrew 578848

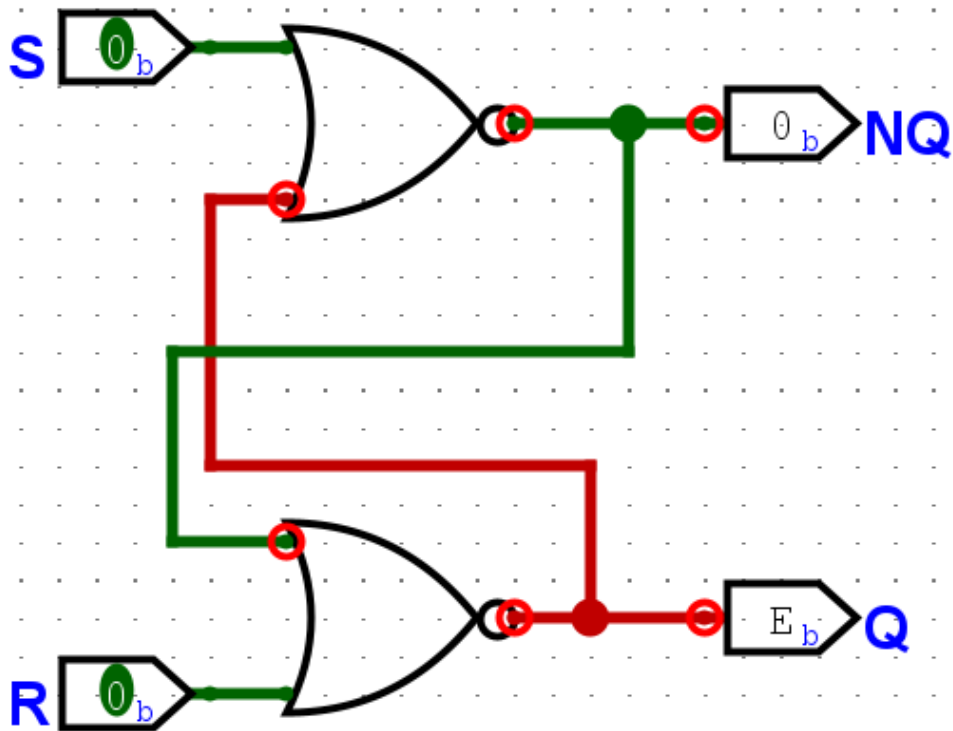

## Assignment 2.6: Vending Machine

Screenshot Vending Machine in Logisim with your name and student number:

Andrew 578848

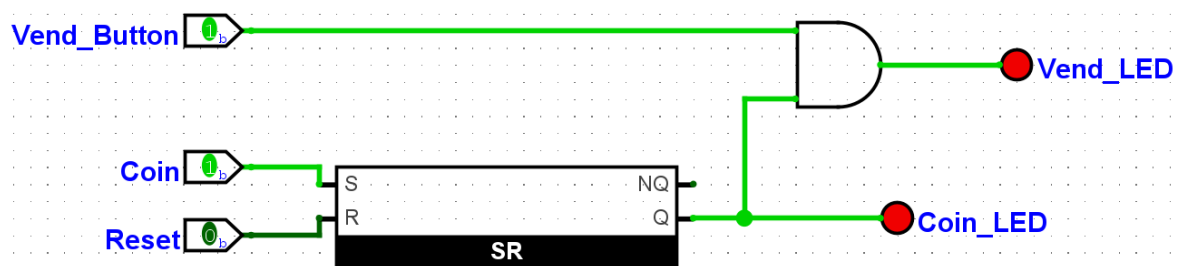

## Assignment 2.7: Bitwise operators

Complete the java source code for bitwise operators. Put the source code here.

```
public class Main {
    static final int READ = 4;
    static final int WRITE = 2;
    static final int EXECUTE = 1;

    public static void main(String[] args) {
        oddOrEven(8);
        oddOrEven(7);

        isPowerOfTwo(2); isPowerOfTwo(1);
        isPowerOfTwo(4); isPowerOfTwo(3);
        isPowerOfTwo(8); isPowerOfTwo(7);
        isPowerOfTwo(16); isPowerOfTwo(15);

        hasPerms(7);
        hasPerms(4);
        hasPerms(2);

        giveWriteAndExecute();
        updatePermissions();

        twoComplement(8);
        twoComplement(-9);
    }

    public static void oddOrEven(Integer number) {
        if ((number & 1) == 1) System.out.println("number " + number + " is odd");
        else System.out.println("number " + number + " is even");
    }

    public static void isPowerOfTwo(Integer number) {
        if((number & (number - 1)) == 0) System.out.println("number " + number + " is a power of 2");
        else System.out.println("number " + number + " isn't a power of 2");
    }
}
```

```

    }

    public static void hasPerms(Integer permission) {
        int userPermissions = permission;

        if ((userPermissions & READ) != 0)
            System.out.println("User with " + permission + " permission has read permissions");
        else
            System.out.println("User with " + permission + " permission can't read. No permissions.");
    }

    public static void giveWriteAndExecute() {
        int userPermissions = WRITE | EXECUTE;
        System.out.println("User permissions: "+userPermissions);
    }

    public static void updatePermissions() {
        int userPermissions = 6;
        int userPermissionsUpdated = userPermissions ^ WRITE;
        System.out.println("User permissions: " + userPermissionsUpdated);
    }

    public static void twoComplement(Integer number) {
        number = ~number + 1;
        System.out.println("Number: " + number);
    }
}

```

### Assignment 2.8: Java Application Bit Calculations

Create a java program that accepts user input and presents a menu with options.

1. Is number odd?
2. Is number a power of 2?
3. Two's complement of number?

Implement the methods by using the bitwise operators you have just learned.

Organize your source code in a readable manner with the use of control flow and methods.

Keep this application because you need to expand it in week 6 for calculating network segments.

Import java.util.Scanner;

```

public class Main {
    static final int READ = 4;
    static final int WRITE = 2;
    static final int EXECUTE = 1;

```

```

public static void main(String[] args) {
    Scanner scanner = new Scanner(System.in);

    System.out.println("1. Is number odd?: ");
    System.out.println("2. Is number a power of 2?: ");
    System.out.println("3. Two's complement of number?: ");

    System.out.println("Select one option by entering a number: ");
    int option = Integer.parseInt(scanner.nextLine());

    System.out.println("Input a number to process: ");
    int number = Integer.parseInt(scanner.nextLine());

    if (option == 1) {
        oddOrEven(number);
    } else if (option == 2) {
        isPowerOfTwo(number);
    } else if (option == 3) {
        twoComplement(3);
    }
}

public static void oddOrEven(Integer number) {
    if ((number & 1) == 1) System.out.println("number " + number + " is odd");
    else System.out.println("number " + number + " is even");
}

public static void isPowerOfTwo(Integer number) {
    if((number & (number - 1)) == 0) System.out.println("number " + number + " is a power of 2");
    else System.out.println("number " + number + " isn't a power of 2");
}

public static void twoComplement(Integer number) {
    number = ~number + 1;
    System.out.println("Number: " + number);
}
}

```

```
1. Is number odd?:  
2. Is number a power of 2?:  
3. Two's complement of number?:  
Select one option by entering a number:  
2  
Input a number to process:  
3  
number 3 isn't a power of 2
```

Paste source code here, with a screenshot of a working application.

Ready? Then save this file and export it as a pdf file with the name: [week2.pdf](#)